

Measurements and Instrumentation [SBE206A] (Fall 2018)

Tutorial 7

Dr. Muhammed Rushdi Asem Alaa

November 26, 2018

Errors during the measurement process

Introduction

- Measurement errors are impossible to avoid.
- we can minimize their magnitude by:
 - good measurement system design.
 - appropriate analysis and processing of measurement data.
- Errors are categorized to:
 - Systematic errors
 - Random errors

Systematic errors

The systematic errors affect the readings in a consistent way, such that all readings are on one side of the true value (either all positive or all negative).

Sources of systematic errors are:

- *Loading error*: system disturbances due to measurement.
- Environmental changes (results in change of sensitivity drift or zero drift).
- *Calibration error*: use of uncalibrated instruments.
- Wear in instruments components (can be compensated by calibration).
- Poor cabling practices.

Random errors

In contrast, random errors have stochastic effects on readings; the readings are distributed around a the true value.

Possible sources of random errors are:

1. Human reading errors.
2. Electrical noise.

| Systematic Error | Random Error |
|------------------|-------------------|
| Poor accuracy | poor precision |
| definite causes | indefinite causes |
| reproducible | not reproducible |

Table 1: Comparison between systematic and random errors

Comparison between systematic and random errors

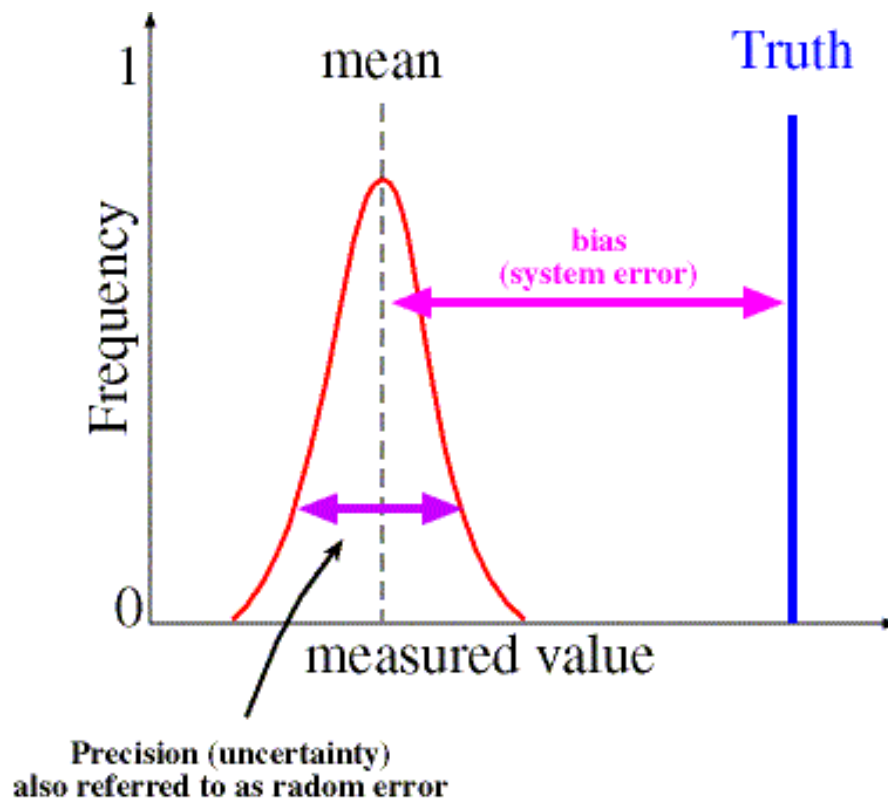


Figure 1: Difference between systematic errors effect and random errors effect.

1. Exercise

Which is more challenging? Systematic errors or random errors?

Aggregation of measurement system errors

The worst-case prediction of maximum error

$$\text{error} = \sum_{i=1}^n x_i \quad (1)$$

Likely maximum systematic error

$$\text{error} = \sqrt{x_1^2 + x_2^2 + \dots + x_n^2} \quad (2)$$

Problems

Systematic Errors

Systematic errors due to disturbance

System Disturbance

2. Exercise

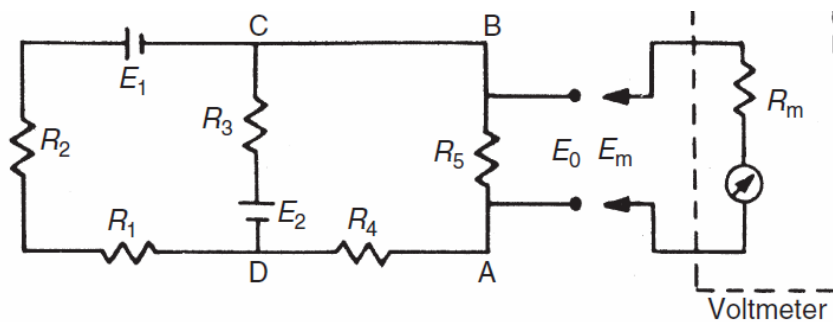


Figure 2: Effect of applying the voltmeter to the measured quantity.

1. Derive the relation of the true and output readings.
2. Suppose that the components of the circuit in Figure 2 have the following values: $R_1 = 400\Omega$, $R_2 = 600\Omega$, $R_3 = 1000\Omega$, $R_4 = 500\Omega$, $R_5 = 1000\Omega$

3. Exercise

An inexpensive voltmeter is used to measure the voltage to within 1 % across the power terminals of a stereo system. Such a system typically has an output impedance of $500\ \Omega$ and a voltage of $120\ \text{V}$ at its power terminals. Assuming that the voltmeter is 100 % accurate such that the instrument and zero-order uncertainties are negligible, determine the minimum input impedance (in Ω) that this voltmeter must have to meet the 1 % criterion.

4. Exercise

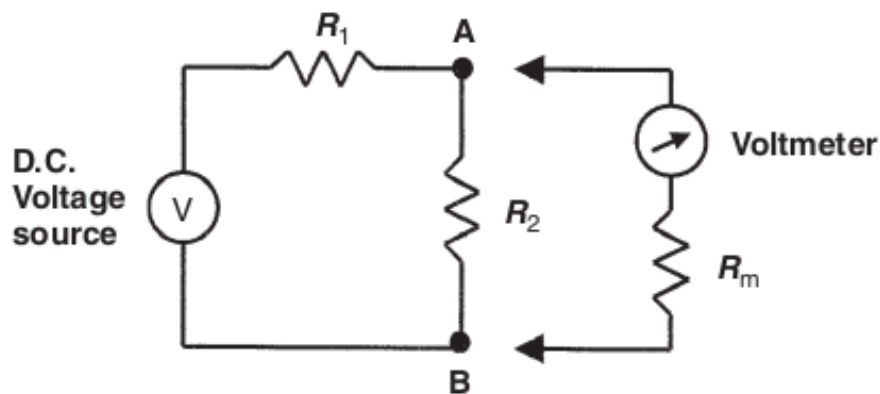


Figure 3: Circuit for Exercise 4

In the circuit shown in Figure 4, the resistor values are given by $R_1 = 1000\ \Omega$; $R_2 = 1000\ \Omega$; $V = 20\ \text{volts}$. The voltage across AB (i.e., across R_2) is measured by a voltmeter whose internal resistance is given by $R_m = 9500\ \Omega$.

1. What will be the reading on the voltmeter?
2. What would the voltage across AB be if the voltmeter was not loading the circuit (i.e., if $R_m = \infty$)?
3. show that the voltage E_m measured across points AB by the voltmeter is related to the true voltage (E_o) by the following expression:

$$\frac{E_m}{E_o} = \frac{R_m(R_1 + R_2)}{R_1(R_2 + R_m) + R_2R_m} \quad (3)$$

4. What is the measurement error due to the loading effect of the voltmeter?
5. If the parameters in Figure 4 have the following values, $R_1 = 5000\Omega$; $R_2 = 10000\Omega$; what value would the voltmeter internal resistance R_m need to be in order not to exceed a measurement error of 1%?

5. Exercise

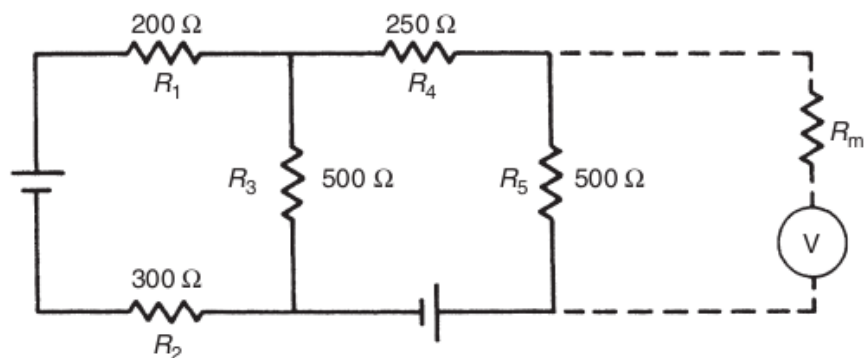


Figure 4: Circuit for Exercise 5

The voltage across a resistance R_5 in the circuit of Figure 5 is to be measured by a voltmeter connected across it.

1. If the voltmeter has an internal resistance (R_m) of 4750Ω , what is the measurement error?
2. What value would the voltmeter internal resistance need to be in order to reduce the measurement error to 1%?

6. Exercise

A requirement for a resistance of 1220Ω in a circuit is satisfied by connecting together resistances of 1000 and 220Ω in series. If each resistance has a tolerance of $\pm 5\%$, what is the likely tolerance in the total resistance?

7. Exercise

In order to calculate the heat loss through the wall of a building, it is necessary to know the temperature difference between inside and outside walls. Temperatures of 5 and 20°C are measured on each side of the wall by mercury-in-glass thermometers with a range of 0 to $\pm 50^\circ\text{C}$ and a quoted inaccuracy of $\pm 1\%$ of full-scale reading.

1. Calculate the likely maximum possible error in the calculated value for the temperature difference.
2. Discuss briefly how using measuring instruments with a different measurement range may improve measurement accuracy.